

Project – SerialControl


Sofiyan Monga


CpE 3020 – VHDL Design with FPGAs


Spring 2022


04/27/2022


Block Diagram:

 

 




 


 

 


Ascii State Diagram:

 


   



Switch State Diagram:

 

Button State Machine:

 

 

 

SerialControl Component Code:

```
-----  
-- SerialControl  
-- Sofiyan Monga  
--  
--     SerialControl takes in a serial input and does various tasks with it.  
--     These tasks include turning any LED on or off, checking the position  
of any  
--     switch, checking which buttons are currently pressed, and outputting  
a  
--     number of the user's choice on the seven-segment display.  
--  
--     These commands are invoked by certain characters being detected by  
the  
--     reciever component, which are L, M, S, B, and D respectively.  
--  
--     A transmitter component is also used to return the position of any  
switch  
--     and for which buttons are pressed.  
--  
-----
```

```
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;
```

```
entity SerialControl is
```

```
    Port ( clock          : in std_logic;  
          rawReset        : in std_logic;  
          serialIn        : in std_logic;  
          upButton        : in std_logic;  
          leftButton      : in std_logic;  
          rightButton     : in std_logic;  
          centerButton    : in std_logic;  
          switches        : in std_logic_vector (15 downto 0);  
          leds            : out std_logic_vector (15 downto 0);  
          segments        : out std_logic_vector (6 downto 0);  
          anodes          : out std_logic_vector (3 downto 0);  
          serialOut       : out std_logic);
```

```
end SerialControl;
```

```
architecture SerialControl_ARCH of SerialControl is
```

```
    --constants-----  
    constant ACTIVE      : std_logic := '1';  
    constant CLOCK_FREQ : integer := 100_000_000;  
    constant BAUD_RATE  : integer := 115_200;  
  
    constant ZERO_BINARY : std_logic_vector(3 downto 0) := "0000";  
    constant ONE_BINARY  : std_logic_vector(3 downto 0) := "0001";  
    constant TWO_BINARY  : std_logic_vector(3 downto 0) := "0010";  
    constant THREE_BINARY: std_logic_vector(3 downto 0) := "0011";  
    constant FOUR_BINARY : std_logic_vector(3 downto 0) := "0100";  
    constant FIVE_BINARY : std_logic_vector(3 downto 0) := "0101";  
    constant SIX_BINARY  : std_logic_vector(3 downto 0) := "0110";  
    constant SEVEN_BINARY: std_logic_vector(3 downto 0) := "0111";
```

```

    constant EIGHT_BINARY: std_logic_vector(3 downto 0) := "1000";
    constant NINE_BINARY : std_logic_vector(3 downto 0) := "1001";

    constant L_ASCII      : std_logic_vector(7 downto 0) :=
"01001100";
    constant M_ASCII      : std_logic_vector(7 downto 0) :=
"01001101";
    constant S_ASCII      : std_logic_vector(7 downto 0) :=
"01010011";
    constant B_ASCII      : std_logic_vector(7 downto 0) :=
"01000010";
    constant D_ASCII      : std_logic_vector(7 downto 0) :=
"01000100";
    constant COMMA_ASCII  : std_logic_vector(7 downto 0) :=
"00101100";

    --arrays for the states below (std_logic_vectors are ASCII-----
-----
    -- Up_a := ('u', 'p', '\n')
    type Up_a is array (0 to 2) of std_logic_vector(7 downto 0);
    signal Up: Up_a := ("01110101", "01110000", COMMA_ASCII);
    -- Down_a := ('d', 'o', 'w', 'n', '\n')
    type Down_a is array (0 to 4) of std_logic_vector(7 downto 0);
    signal Down: Down_a := ("01100100", "01101111", "01110111", "01101110",
COMMA_ASCII);
    -- Right_a := ('r', 'i', 'g', 'h', 't', '\n')
    type Right_a is array (0 to 5) of std_logic_vector(7 downto 0);
    signal Right: Right_a := ("01110010", "01101001", "01100111", "01101000",
"01110100", COMMA_ASCII);
    -- Left_a := ('l', 'e', 'f', 't', '\n')
    type Left_a is array (0 to 4) of std_logic_vector(7 downto 0);
    signal Left: Left_a := ("01101100", "01100101", "01100110", "01110100",
COMMA_ASCII);
    -- Center_a := ('c', 'e', 'n', 't', 'e', 'r', '\n')
    type Center_a is array (0 to 6) of std_logic_vector(7 downto 0);
    signal Center: Center_a := ("01100011", "01100101", "01101110",
"01110100", "01100101", "01110010", COMMA_ASCII);

    --ascii state declaration-----
--
    type Ascii_t is (WAIT_FOR_COMMAND, BUTTON_COMMAND,
SEG_WAIT_FOR_FIRST_DIGIT, SEG_FIRST_DIGIT_RECEIVED,
                        SEG_WAIT_FOR_SECOND_DIGIT, SEG_SECOND_DIGIT_RECEIVED,
SEG_WAIT_FOR_THIRD_DIGIT,
                        SEG_THIRD_DIGIT_RECEIVED, SEG_WAIT_FOR_FOURTH_DIGIT,
SEG_FOURTH_DIGIT_RECEIVED,
                        SWITCH_WAIT_FOR_FIRST_DIGIT,
SWITCH_FIRST_DIGIT_RECEIVED, SWITCH_WAIT_FOR_SECOND_DIGIT,
                        SWITCH_SECOND_DIGIT_RECEIVED,
OFF_LED_WAIT_FOR_FIRST_DIGIT, OFF_LED_FIRST_DIGIT_RECEIVED,
                        OFF_LED_WAIT_FOR_SECOND_DIGIT,
OFF_LED_SECOND_DIGIT_RECEIVED, ON_LED_WAIT_FOR_FIRST_DIGIT,
                        ON_LED_FIRST_DIGIT_RECEIVED,
ON_LED_WAIT_FOR_SECOND_DIGIT, ON_LED_SECOND_DIGIT_RECEIVED, PULSE_SEG,
                        PULSE_ON_LED, PULSE_OFF_LED, SWITCH_COMMAND);

    signal currentAsciiState: Ascii_t;
    signal nextAsciiState  : Ascii_t;

```

```

--switch state declaration-----
type Switch_t is (WAIT_FOR_SWITCH_CONTROL, CHECK_SWITCH_STATE,
TRANSMIT_FIRST_UP_CHAR, WAIT_FOR_FIRST_UP_TX_COMPLETE,
                    TRANSMIT_SECOND_UP_CHAR,
WAIT_FOR_SECOND_UP_TX_COMPLETE, TRANSMIT_THIRD_UP_CHAR,
                    WAIT_FOR_THIRD_UP_TX_COMPLETE,
TRANSMIT_FIRST_DOWN_CHAR, WAIT_FOR_FIRST_DOWN_TX_COMPLETE,
                    TRANSMIT_SECOND_DOWN_CHAR,
WAIT_FOR_SECOND_DOWN_TX_COMPLETE, TRANSMIT_THIRD_DOWN_CHAR,
                    WAIT_FOR_THIRD_DOWN_TX_COMPLETE,
TRANSMIT_FOURTH_DOWN_CHAR, WAIT_FOR_FOURTH_DOWN_TX_COMPLETE,
                    TRANSMIT_FIFTH_DOWN_CHAR,
WAIT_FOR_FIFTH_DOWN_TX_COMPLETE, SWITCH_TX_FINISHED);
signal currentSwitchState: Switch_t;
signal nextSwitchState   : Switch_t;

--button state declaration-----
type Button_t is (WAIT_FOR_BUTTON_CONTROL, CHECK_UP_BUTTON,
TRANSMIT_FIRST_UP, WAIT_AFTER_FIRST_UP, TRANSMIT_SECOND_UP,
                    WAIT_AFTER_SECOND_UP, TRANSMIT_THIRD_UP,
WAIT_AFTER_THIRD_UP, CHECK_LEFT_BUTTON, TRANSMIT_FIRST_LEFT,
                    WAIT_AFTER_FIRST_LEFT, TRANSMIT_SECOND_LEFT,
WAIT_AFTER_SECOND_LEFT, TRANSMIT_THIRD_LEFT,
                    WAIT_AFTER_THIRD_LEFT, TRANSMIT_FOURTH_LEFT,
WAIT_AFTER_FOURTH_LEFT, TRANSMIT_FIFTH_LEFT,
                    WAIT_AFTER_FIFTH_LEFT, CHECK_RIGHT_BUTTON,
TRANSMIT_FIRST_RIGHT, WAIT_AFTER_FIRST_RIGHT,
                    TRANSMIT_SECOND_RIGHT, WAIT_AFTER_SECOND_RIGHT,
TRANSMIT_THIRD_RIGHT, WAIT_AFTER_THIRD_RIGHT,
                    TRANSMIT_FOURTH_RIGHT, WAIT_AFTER_FOURTH_RIGHT,
TRANSMIT_FIFTH_RIGHT, WAIT_AFTER_FIFTH_RIGHT,
                    TRANSMIT_SIXTH_RIGHT, WAIT_AFTER_SIXTH_RIGHT,
CHECK_CENTER_BUTTON, TRANSMIT_FIRST_CENTER,
                    WAIT_AFTER_FIRST_CENTER, TRANSMIT_SECOND_CENTER,
WAIT_AFTER_SECOND_CENTER, TRANSMIT_THIRD_CENTER,
                    WAIT_AFTER_THIRD_CENTER, TRANSMIT_FOURTH_CENTER,
WAIT_AFTER_FOURTH_CENTER, TRANSMIT_FIFTH_CENTER,
                    WAIT_AFTER_FIFTH_CENTER, TRANSMIT_SIXTH_CENTER,
WAIT_AFTER_SIXTH_CENTER, TRANSMIT_SEVENTH_CENTER,
                    WAIT_AFTER_SEVENTH_CENTER, BUTTON_TX_FINISHED);
signal currentButtonState: Button_t;
signal nextButtonState   : Button_t;

--SevenSegmentDriver component-----
component SevenSegmentDriver
port(
    reset: in std_logic;
    clock: in std_logic;

    digit3: in std_logic_vector(3 downto 0);    --leftmost digit
    digit2: in std_logic_vector(3 downto 0);    --2nd from left digit
    digit1: in std_logic_vector(3 downto 0);    --3rd from left digit
    digit0: in std_logic_vector(3 downto 0);    --rightmost digit

    blank3: in std_logic;    --leftmost digit
    blank2: in std_logic;    --2nd from left digit

```

```

        blank1: in std_logic;    --3rd from left digit
        blank0: in std_logic;    --rightmost digit

        sevenSegs: out std_logic_vector(6 downto 0);    --MSB=g, LSB=a
        anodes:    out std_logic_vector(3 downto 0)    --MSB=leftmost
digit
    );
end component;

--SynchronizerChain component-----
component SynchronizerChain is
    generic (CHAIN_SIZE: positive);
    port (
        reset:    in  std_logic;
        clock:    in  std_logic;
        asyncIn:  in  std_logic;
        syncOut:  out std_logic
    );
end component;

--UartRx component-----
component UartRx is
    generic (
        BAUD_RATE:  positive;
        CLOCK_FREQ: positive
    );
    port (
        clock: in std_logic;
        reset: in std_logic;
        rxData: in std_logic;
        dataReady: out std_logic;
        dataOut: out std_logic_vector(7 downto 0)
    );
end component;

--UartTx component-----
component UartTx is
    generic(
        BAUD_RATE:  positive;
        CLOCK_FREQ: positive
    );
    port(
        clock:    in  std_logic;
        reset:    in  std_logic;
        txEn:     in  std_logic;
        dataIn:    in  std_logic_vector(7 downto 0);
        txComplete: out std_logic;
        dataOut:   out std_logic
    );
end component;

--other internal signals-----
signal convertEn      : std_logic;
signal buttonTxFinished: std_logic;
signal switchTxFinished: std_logic;
signal ledOffEn       : std_logic;
signal ledOnEn        : std_logic;

```

```

signal buttonControl    : std_logic;
signal segEn            : std_logic;
signal switchControl    : std_logic;
signal digit01En        : std_logic;
signal digit02En        : std_logic;
signal digit03En        : std_logic;
signal digit04En        : std_logic;
signal txEn             : std_logic;
signal centerButtonSync : std_logic;
signal rightButtonSync  : std_logic;
signal leftButtonSync   : std_logic;
signal upButtonSync     : std_logic;
signal buttonTxEn       : std_logic;
signal txComplete       : std_logic;
signal switchTxEn       : std_logic;
signal reset            : std_logic;
signal userNum          : integer range 0 to 16;
signal digit1           : std_logic_vector (3 downto 0);
signal digit2           : std_logic_vector (3 downto 0);
signal digit3           : std_logic_vector (3 downto 0);
signal digit4           : std_logic_vector (3 downto 0);
signal segDigit0        : std_logic_vector (3 downto 0);
signal segDigit1        : std_logic_vector (3 downto 0);
signal segDigit2        : std_logic_vector (3 downto 0);
signal segDigit3        : std_logic_vector (3 downto 0);
signal switchChar       : std_logic_vector (7 downto 0);
signal buttonChar       : std_logic_vector (7 downto 0);
signal charToSend       : std_logic_vector (7 downto 0);
signal myChar           : std_logic_vector (7 downto 0);

```

begin

```

--port map for SevenSegmentDriver-----
SEGMENT_DRIVER: SevenSegmentDriver

```

```

    port map (
        clock      => clock,
        reset      => reset,
        digit3     => segDigit3,
        digit2     => segDigit2,
        digit1     => segDigit1,
        digit0     => segDigit0,
        blank3     => not ACTIVE,
        blank2     => not ACTIVE,
        blank1     => not ACTIVE,
        blank0     => not ACTIVE,
        sevenSegs  => segments,
        anodes     => anodes
    );

```

```

--port map for SynchronizerChain-----
UP_BUTTON_SYNC: SynchronizerChain

```

```

    generic map (
        CHAIN_SIZE => 2
    )
    port map (
        reset      => reset,
        clock      => clock,
        asyncIn    => upButton,

```

```

        syncOut => upButtonSync
    );

--port map for SynchronizerChain-----
LEFT_BUTTON_SYNC: SynchronizerChain
    generic map (
        CHAIN_SIZE => 2
    )
    port map (
        reset    => reset,
        clock     => clock,
        asyncIn   => leftButton,
        syncOut   => leftButtonSync
    );

--port map for SynchronizerChain-----
RIGHT_BUTTON_SYNC: SynchronizerChain
    generic map (
        CHAIN_SIZE => 2
    )
    port map (
        reset    => reset,
        clock     => clock,
        asyncIn   => rightButton,
        syncOut   => rightButtonSync
    );

--port map for SynchronizerChain-----
CENTER_BUTTON_SYNC: SynchronizerChain
    generic map (
        CHAIN_SIZE => 2
    )
    port map (
        reset    => reset,
        clock     => clock,
        asyncIn   => centerButton,
        syncOut   => centerButtonSync
    );

--port map for UartRx-----
MY_RECEIVER: UartRx
    generic map (
        BAUD_RATE => BAUD_RATE,
        CLOCK_FREQ => CLOCK_FREQ
    )
    port map (
        reset      => reset,
        clock       => clock,
        rxData      => serialIn,
        dataOut     => myChar,
        dataReady   => convertEn
    );

--port map for UartTx-----
MY_TRANSMITTER: UartTx
    generic map (
        BAUD_RATE => BAUD_RATE,

```

```

        CLOCK_FREQ => CLOCK_FREQ
    )
    port map (
        reset      => reset,
        clock       => clock,
        txEn        => txEn,
        dataIn       => charToSend,
        dataOut      => serialOut,
        txComplete  => txComplete
    );

--synchronize reset signal to end on a clock edge-----
---
RESET_SYNCHRONIZER: process (rawReset, clock)
    variable chain: std_logic_vector(1 downto 0);
begin
    if (rawReset = ACTIVE) then
        chain := (others => ACTIVE);
    elsif (rising_edge(clock)) then
        chain := chain(0) & not ACTIVE;
    end if;
    reset <= chain(1);
end process RESET_SYNCHRONIZER;

--state register for ASCII_TRANSITION-----
---
ASCII_REGISTER: process (reset, clock)
begin
    if (reset = ACTIVE) then
        currentAsciiState <= WAIT_FOR_COMMAND;
    elsif (rising_edge(clock)) then
        currentAsciiState <= nextAsciiState;
    end if;
end process ASCII_REGISTER;

--state transition block for the Ascii State Machine-----
-----
ASCII_TRANSITION: process (myChar, buttonTxFinished, switchTxFinished,
convertEn, currentAsciiState)
begin
    --default values for outputs-----
    -
    ledOffEn      <= not ACTIVE;
    ledOnEn       <= not ACTIVE;
    buttonControl <= not ACTIVE;
    segEn         <= not ACTIVE;
    switchControl <= not ACTIVE;
    digit01En     <= not ACTIVE;
    digit02En     <= not ACTIVE;
    digit03En     <= not ACTIVE;
    digit04En     <= not ACTIVE;

    case currentAsciiState is

        --WAIT_FOR_COMMAND state-----
        -
        when WAIT_FOR_COMMAND =>

```

```

ledOffEn      <= not ACTIVE;
ledOnEn       <= not ACTIVE;
buttonControl <= not ACTIVE;
segEn         <= not ACTIVE;
switchControl <= not ACTIVE;
digit01En     <= not ACTIVE;
digit02En     <= not ACTIVE;
digit03En     <= not ACTIVE;
digit04En     <= not ACTIVE;

if (convertEn = ACTIVE) then
    if (myChar = B_ASCII) then
        nextAsciiState <= BUTTON_COMMAND;
    elsif (myChar = D_ASCII) then
        nextAsciiState <= SEG_WAIT_FOR_FIRST_DIGIT;
    elsif (myChar = S_ASCII) then
        nextAsciiState <= SWITCH_WAIT_FOR_FIRST_DIGIT;
    elsif (myChar = M_ASCII) then
        nextAsciiState <= OFF_LED_WAIT_FOR_FIRST_DIGIT;
    elsif (myChar = L_ASCII) then
        nextAsciiState <= ON_LED_WAIT_FOR_FIRST_DIGIT;
    end if;
else
    nextAsciiState <= WAIT_FOR_COMMAND;
end if;

--BUTTON_CONTROL state-----
when BUTTON_COMMAND =>
    buttonControl <= ACTIVE;

    if (buttonTxFinished = ACTIVE) then
        nextAsciiState <= WAIT_FOR_COMMAND;
    else
        nextAsciiState <= BUTTON_COMMAND;
    end if;

--Segment section of the Ascii State Machine-----
--SEG_WAIT_FOR_FIRST_DIGIT-----
when SEG_WAIT_FOR_FIRST_DIGIT =>
    if (convertEn = ACTIVE) then
        nextAsciiState <= SEG_FIRST_DIGIT_RECEIVED;
    else
        nextAsciiState <= SEG_WAIT_FOR_FIRST_DIGIT;
    end if;

--SEG_FIRST_DIGIT_RECEIVED-----
when SEG_FIRST_DIGIT_RECEIVED =>
    digit04En <= ACTIVE;
    nextAsciiState <= SEG_WAIT_FOR_SECOND_DIGIT;

--SEG_WAIT_FOR_SECOND_DIGIT-----
when SEG_WAIT_FOR_SECOND_DIGIT =>
    if (convertEn = ACTIVE) then
        nextAsciiState <= SEG_SECOND_DIGIT_RECEIVED;
    else
        nextAsciiState <= SEG_WAIT_FOR_SECOND_DIGIT;

```

```

        end if;

--SEG_SECOND_DIGIT_RECEIVED-----
when SEG_SECOND_DIGIT_RECEIVED =>
    digit03En <= ACTIVE;
    nextAsciiState <= SEG_WAIT_FOR_THIRD_DIGIT;

--SEG_WAIT_FOR_THIRD_DIGIT-----
when SEG_WAIT_FOR_THIRD_DIGIT =>
    if (convertEn = ACTIVE) then
        nextAsciiState <= SEG_THIRD_DIGIT_RECEIVED;
    else
        nextAsciiState <= SEG_WAIT_FOR_THIRD_DIGIT;
    end if;

--SEG_THIRD_DIGIT_RECEIVED-----
when SEG_THIRD_DIGIT_RECEIVED =>
    digit02En <= ACTIVE;
    nextAsciiState <= SEG_WAIT_FOR_FOURTH_DIGIT;

--SEG_WAIT_FOR_FOURTH_DIGIT-----
when SEG_WAIT_FOR_FOURTH_DIGIT =>
    if (convertEn = ACTIVE) then
        nextAsciiState <= SEG_FOURTH_DIGIT_RECEIVED;
    else
        nextAsciiState <= SEG_WAIT_FOR_FOURTH_DIGIT;
    end if;

--SEG_FOURTH_DIGIT_RECEIVED-----
when SEG_FOURTH_DIGIT_RECEIVED =>
    digit01En <= ACTIVE;
    nextAsciiState <= PULSE_SEG;

--PULSE_SEG-----
when PULSE_SEG =>
    segen <= ACTIVE;
    nextAsciiState <= WAIT_FOR_COMMAND;

--Switch section of the Ascii State Machine-----
--SWITCH_WAIT_FOR_FIRST_DIGIT-----
when SWITCH_WAIT_FOR_FIRST_DIGIT =>
    if (convertEn = ACTIVE) then
        nextAsciiState <= SWITCH_FIRST_DIGIT_RECEIVED;
    else
        nextAsciiState <= SWITCH_WAIT_FOR_FIRST_DIGIT;
    end if;

--SWITCH_FIRST_DIGIT_RECEIVED-----
when SWITCH_FIRST_DIGIT_RECEIVED =>
    digit02En <= ACTIVE;
    nextAsciiState <= SWITCH_WAIT_FOR_SECOND_DIGIT;

--SWITCH_WAIT_FOR_SECOND_DIGIT-----
when SWITCH_WAIT_FOR_SECOND_DIGIT =>
    if (convertEn = ACTIVE) then
        nextAsciiState <= SWITCH_SECOND_DIGIT_RECEIVED;
    else

```

```

        nextAsciiState <= SWITCH_WAIT_FOR_SECOND_DIGIT;
    end if;

--SWITCH_SECOND_DIGIT_RECEIVED-----
when SWITCH_SECOND_DIGIT_RECEIVED =>
    digit01En <= ACTIVE;
    nextAsciiState <= SWITCH_COMMAND;

--SWITCH_COMMAND-----
when SWITCH_COMMAND =>
    switchControl <= ACTIVE;

    if (switchTxFinished = ACTIVE) then
        nextAsciiState <= WAIT_FOR_COMMAND;
    else
        nextAsciiState <= SWITCH_COMMAND;
    end if;

--LED OFF section of the Ascii State Machine-----
--OFF_LED_WAIT_FOR_FIRST_DIGIT-----
when OFF_LED_WAIT_FOR_FIRST_DIGIT =>
    if (convertEn = ACTIVE) then
        nextAsciiState <= OFF_LED_FIRST_DIGIT_RECEIVED;
    else
        nextAsciiState <= OFF_LED_WAIT_FOR_FIRST_DIGIT;
    end if;

--OFF_LED_FIRST_DIGIT_RECEIVED-----
when OFF_LED_FIRST_DIGIT_RECEIVED =>
    digit02En <= ACTIVE;
    nextAsciiState <= OFF_LED_WAIT_FOR_SECOND_DIGIT;

--OFF_LED_WAIT_FOR_SECOND_DIGIT-----
when OFF_LED_WAIT_FOR_SECOND_DIGIT =>
    if (convertEn = ACTIVE) then
        nextAsciiState <= OFF_LED_SECOND_DIGIT_RECEIVED;
    else
        nextAsciiState <= OFF_LED_WAIT_FOR_SECOND_DIGIT;
    end if;

--OFF_LED_SECOND_DIGIT_RECEIVED-----
when OFF_LED_SECOND_DIGIT_RECEIVED =>
    digit01En <= ACTIVE;
    nextAsciiState <= PULSE_OFF_LED;

--PULSE_OFF_LED-----
when PULSE_OFF_LED =>
    ledOffEn <= ACTIVE;
    nextAsciiState <= WAIT_FOR_COMMAND;

--LED ON section of the Ascii State Machine-----
--ON_LED_WAIT_FOR_FIRST_DIGIT-----
when ON_LED_WAIT_FOR_FIRST_DIGIT =>
    if (convertEn = ACTIVE) then
        nextAsciiState <= ON_LED_FIRST_DIGIT_RECEIVED;

```

```

        else
            nextAsciiState <= ON_LED_WAIT_FOR_FIRST_DIGIT;
        end if;

--ON_LED_FIRST_DIGIT_RECEIVED-----
when ON_LED_FIRST_DIGIT_RECEIVED =>
    digit02En <= ACTIVE;
    nextAsciiState <= ON_LED_WAIT_FOR_SECOND_DIGIT;

--ON_LED_WAIT_FOR_SECOND_DIGIT-----
when ON_LED_WAIT_FOR_SECOND_DIGIT =>
    if (convertEn = ACTIVE) then
        nextAsciiState <= ON_LED_SECOND_DIGIT_RECEIVED;
    else
        nextAsciiState <= ON_LED_WAIT_FOR_SECOND_DIGIT;
    end if;

--ON_LED_SECOND_DIGIT_RECEIVED-----
when ON_LED_SECOND_DIGIT_RECEIVED =>
    digit01En <= ACTIVE;
    nextAsciiState <= PULSE_ON_LED;

--PULSE_ON_LED-----
when PULSE_ON_LED =>
    ledOnEn <= ACTIVE;
    nextAsciiState <= WAIT_FOR_COMMAND;

    end case;
end process ASCII_TRANSITION;

--state register for SWITCH_SHIFT_TRANSITION-----
SWITCH_STATE_REGISTER: process (reset, clock)
begin
    if (reset = ACTIVE) then
        currentSwitchState <= WAIT_FOR_SWITCH_CONTROL;
    elsif (rising_edge(clock)) then
        currentSwitchState <= nextSwitchState;
    end if;
end process SWITCH_STATE_REGISTER;

--state transition block for the Switch State Machine-----
SWITCH_SHIFT_TRANSITION: process (switches, txComplete, userNum,
switchControl, currentSwitchState)
begin
    --default values for outputs-----
    switchTxEn <= not ACTIVE;
    switchChar <= (others => not ACTIVE);
    switchTxFinished <= not ACTIVE;

    case currentSwitchState is

        --WAIT_FOR_SWITCH_CONTROL-----
        when WAIT_FOR_SWITCH_CONTROL =>
            switchTxEn <= not ACTIVE;
            switchChar <= (others => not ACTIVE);
            switchTxFinished <= not ACTIVE;

```

```

    if (switchControl = ACTIVE) then
        nextSwitchState <= CHECK_SWITCH_STATE;
    else
        nextSwitchState <= WAIT_FOR_SWITCH_CONTROL;
    end if;

--CHECK_SWITCH_STATE-----
when CHECK_SWITCH_STATE =>
    if (switches(userNum) = ACTIVE) then
        nextSwitchState <= TRANSMIT_FIRST_UP_CHAR;
    else
        nextSwitchState <= TRANSMIT_FIRST_DOWN_CHAR;
    end if;

--TRANSMIT_FIRST_UP_CHAR-----
when TRANSMIT_FIRST_UP_CHAR =>
    switchChar <= Up(0);
    switchTxEn <= ACTIVE;
    nextSwitchState <= WAIT_FOR_FIRST_UP_TX_COMPLETE;

--WAIT_FOR_FIRST_UP_TX_COMPLETE-----
when WAIT_FOR_FIRST_UP_TX_COMPLETE =>
    if (txComplete = ACTIVE) then
        nextSwitchState <= TRANSMIT_SECOND_UP_CHAR;
    else
        nextSwitchState <= WAIT_FOR_FIRST_UP_TX_COMPLETE;
    end if;

--TRANSMIT_SECOND_UP_CHAR-----
when TRANSMIT_SECOND_UP_CHAR =>
    switchChar <= Up(1);
    switchTxEn <= ACTIVE;
    nextSwitchState <= WAIT_FOR_SECOND_UP_TX_COMPLETE;

--WAIT_FOR_SECOND_UP_TX_COMPLETE-----
when WAIT_FOR_SECOND_UP_TX_COMPLETE =>
    if (txComplete = ACTIVE) then
        nextSwitchState <= TRANSMIT_THIRD_UP_CHAR;
    else
        nextSwitchState <= WAIT_FOR_SECOND_UP_TX_COMPLETE;
    end if;

--TRANSMIT_THIRD_UP_CHAR-----
when TRANSMIT_THIRD_UP_CHAR =>
    switchChar <= Up(2);
    switchTxEn <= ACTIVE;
    nextSwitchState <= WAIT_FOR_THIRD_UP_TX_COMPLETE;

--WAIT_FOR_THIRD_UP_TX_COMPLETE-----
when WAIT_FOR_THIRD_UP_TX_COMPLETE =>
    if (txComplete = ACTIVE) then
        nextSwitchState <= SWITCH_TX_FINISHED;
    else
        nextSwitchState <= WAIT_FOR_THIRD_UP_TX_COMPLETE;
    end if;

```

```

--TRANSMIT_FIRST_DOWN_CHAR-----
when TRANSMIT_FIRST_DOWN_CHAR =>
    switchChar <= Down(0);
    switchTxEn <= ACTIVE;
    nextSwitchState <= WAIT_FOR_FIRST_DOWN_TX_COMPLETE;

--WAIT_FOR_FIRST_DOWN_TX_COMPLETE-----
when WAIT_FOR_FIRST_DOWN_TX_COMPLETE =>
    if (txComplete = ACTIVE) then
        nextSwitchState <= TRANSMIT_SECOND_DOWN_CHAR;
    else
        nextSwitchState <= WAIT_FOR_FIRST_DOWN_TX_COMPLETE;
    end if;

--TRANSMIT_SECOND_DOWN_CHAR-----
when TRANSMIT_SECOND_DOWN_CHAR =>
    switchChar <= Down(1);
    switchTxEn <= ACTIVE;
    nextSwitchState <= WAIT_FOR_SECOND_DOWN_TX_COMPLETE;

--WAIT_FOR_SECOND_DOWN_TX_COMPLETE-----
when WAIT_FOR_SECOND_DOWN_TX_COMPLETE =>
    if (txComplete = ACTIVE) then
        nextSwitchState <= TRANSMIT_THIRD_DOWN_CHAR;
    else
        nextSwitchState <= WAIT_FOR_SECOND_DOWN_TX_COMPLETE;
    end if;

--TRANSMIT_THIRD_DOWN_CHAR-----
when TRANSMIT_THIRD_DOWN_CHAR =>
    switchChar <= Down(2);
    switchTxEn <= ACTIVE;
    nextSwitchState <= WAIT_FOR_THIRD_DOWN_TX_COMPLETE;

--WAIT_FOR_THIRD_DOWN_TX_COMPLETE-----
when WAIT_FOR_THIRD_DOWN_TX_COMPLETE =>
    if (txComplete = ACTIVE) then
        nextSwitchState <= TRANSMIT_FOURTH_DOWN_CHAR;
    else
        nextSwitchState <= WAIT_FOR_THIRD_DOWN_TX_COMPLETE;
    end if;

--TRANSMIT_FOURTH_DOWN_CHAR-----
when TRANSMIT_FOURTH_DOWN_CHAR =>
    switchChar <= Down(3);
    switchTxEn <= ACTIVE;
    nextSwitchState <= WAIT_FOR_FOURTH_DOWN_TX_COMPLETE;

--WAIT_FOR_FOURTH_DOWN_TX_COMPLETE-----
when WAIT_FOR_FOURTH_DOWN_TX_COMPLETE =>
    if (txComplete = ACTIVE) then
        nextSwitchState <= TRANSMIT_FIFTH_DOWN_CHAR;
    else
        nextSwitchState <= WAIT_FOR_FOURTH_DOWN_TX_COMPLETE;
    end if;

--TRANSMIT_FIFTH_DOWN_CHAR-----

```

```

when TRANSMIT_FIFTH_DOWN_CHAR =>
    switchChar <= Down(4);
    switchTxEn <= ACTIVE;
    nextSwitchState <= WAIT_FOR_FIFTH_DOWN_TX_COMPLETE;

--WAIT_FOR_FIFTH_DOWN_TX_COMPLETE-----
when WAIT_FOR_FIFTH_DOWN_TX_COMPLETE =>
    if (txComplete = ACTIVE) then
        nextSwitchState <= SWITCH_TX_FINISHED;
    else
        nextSwitchState <= WAIT_FOR_FIFTH_DOWN_TX_COMPLETE;
    end if;

--SWITCH_TX_FINISHED-----
when SWITCH_TX_FINISHED =>
    switchTxFinished <= ACTIVE;
    nextSwitchState <= WAIT_FOR_SWITCH_CONTROL;
end case;
end process SWITCH_SHIFT_TRANSITION;

--state register for BUTTON_STATE_TRANSITION-----
BUTTON_STATE_REGISTER: process (reset, clock)
begin
    if (reset = ACTIVE) then
        currentButtonState <= WAIT_FOR_BUTTON_CONTROL;
    elsif (rising_edge(clock)) then
        currentButtonState <= nextButtonState;
    end if;
end process BUTTON_STATE_REGISTER;

--state transition for the Button State Machine-----
--
    BUTTON_STATE_TRANSITION: process (buttonControl, upButtonSync,
leftButtonSync, rightButtonSync, centerButtonSync, txComplete,
currentButtonState)
begin
    --default value for the outputs-----
    buttonTxEn <= not ACTIVE;
    buttonChar <= (others => not ACTIVE);
    buttonTxFinished <= not ACTIVE;

    case currentButtonState is

        --WAIT_FOR_BUTTON_CONTROL-----
        when WAIT_FOR_BUTTON_CONTROL =>
            buttonTxEn <= not ACTIVE;
            buttonChar <= (others => not ACTIVE);
            buttonTxFinished <= not ACTIVE;

            if (buttonControl = ACTIVE) then
                nextButtonState <= CHECK_UP_BUTTON;
            else
                nextButtonState <= WAIT_FOR_BUTTON_CONTROL;
            end if;

            --CHECK_UP_BUTTON-----
            when CHECK_UP_BUTTON =>

```

```

    if (upButtonSync = ACTIVE) then
        nextButtonState <= TRANSMIT_FIRST_UP;
    else
        nextButtonState <= CHECK_LEFT_BUTTON;
    end if;

--TRANSMIT_FIRST_UP-----
when TRANSMIT_FIRST_UP =>
    buttonChar <= Up(0);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_FIRST_UP;

--WAIT_AFTER_FIRST_UP-----
when WAIT_AFTER_FIRST_UP =>
    if (txComplete = ACTIVE) then
        nextButtonState <= TRANSMIT_SECOND_UP;
    else
        nextButtonState <= WAIT_AFTER_FIRST_UP;
    end if;

--TRANSMIT_SECOND_UP-----
when TRANSMIT_SECOND_UP =>
    buttonChar <= Up(1);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_SECOND_UP;

--WAIT_AFTER_SECOND_UP-----
when WAIT_AFTER_SECOND_UP =>
    if (txComplete = ACTIVE) then
        nextButtonState <= TRANSMIT_THIRD_UP;
    else
        nextButtonState <= WAIT_AFTER_SECOND_UP;
    end if;

--TRANSMIT_THIRD_UP-----
when TRANSMIT_THIRD_UP =>
    buttonChar <= Up(2);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_THIRD_UP;

--WAIT_AFTER_THIRD_UP-----
when WAIT_AFTER_THIRD_UP =>
    if (txComplete = ACTIVE) then
        nextButtonState <= CHECK_LEFT_BUTTON;
    else
        nextButtonState <= WAIT_AFTER_THIRD_UP;
    end if;

--CHECK_LEFT_BUTTON-----
when CHECK_LEFT_BUTTON =>
    if (leftButtonSync = ACTIVE) then
        nextButtonState <= TRANSMIT_FIRST_LEFT;
    else
        nextButtonState <= CHECK_RIGHT_BUTTON;
    end if;

--TRANSMIT_FIRST_LEFT-----

```

```

when TRANSMIT_FIRST_LEFT =>
    buttonChar <= Left(0);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_FIRST_LEFT;

--WAIT_AFTER_FIRST_LEFT-----
when WAIT_AFTER_FIRST_LEFT =>
    if (txComplete = ACTIVE) then
        nextButtonState <= TRANSMIT_SECOND_LEFT;
    else
        nextButtonState <= WAIT_AFTER_FIRST_LEFT;
    end if;

--TRANSMIT_SECOND_LEFT-----
when TRANSMIT_SECOND_LEFT =>
    buttonChar <= Left(1);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_SECOND_LEFT;

--WAIT_AFTER_SECOND_LEFT-----
when WAIT_AFTER_SECOND_LEFT =>
    if (txComplete = ACTIVE) then
        nextButtonState <= TRANSMIT_THIRD_LEFT;
    else
        nextButtonState <= WAIT_AFTER_SECOND_LEFT;
    end if;

--TRANSMIT_THIRD_LEFT-----
when TRANSMIT_THIRD_LEFT =>
    buttonChar <= Left(2);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_THIRD_LEFT;

--WAIT_AFTER_THIRD_LEFT-----
when WAIT_AFTER_THIRD_LEFT =>
    if (txComplete = ACTIVE) then
        nextButtonState <= TRANSMIT_FOURTH_LEFT;
    else
        nextButtonState <= WAIT_AFTER_THIRD_LEFT;
    end if;

--TRANSMIT_FOURTH_LEFT-----
when TRANSMIT_FOURTH_LEFT =>
    buttonChar <= Left(3);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_FOURTH_LEFT;

--WAIT_AFTER_FOURTH_LEFT-----
when WAIT_AFTER_FOURTH_LEFT =>
    if (txComplete = ACTIVE) then
        nextButtonState <= TRANSMIT_FIFTH_LEFT;
    else
        nextButtonState <= WAIT_AFTER_FOURTH_LEFT;
    end if;

--TRANSMIT_FIFTH_LEFT-----
when TRANSMIT_FIFTH_LEFT =>

```

```

buttonChar <= Left(4);
buttonTxEn <= ACTIVE;
nextButtonState <= WAIT_AFTER_FIFTH_LEFT;

--WAIT_AFTER_FIFTH_LEFT-----
when WAIT_AFTER_FIFTH_LEFT =>
    if (txComplete = ACTIVE) then
        nextButtonState <= CHECK_RIGHT_BUTTON;
    else
        nextButtonState <= WAIT_AFTER_FIFTH_LEFT;
    end if;

--CHECK_RIGHT_BUTTON-----
when CHECK_RIGHT_BUTTON =>
    if (rightButtonSync = ACTIVE) then
        nextButtonState <= TRANSMIT_FIRST_RIGHT;
    else
        nextButtonState <= CHECK_CENTER_BUTTON;
    end if;

--TRANSMIT_FIRST_RIGHT-----
when TRANSMIT_FIRST_RIGHT =>
    buttonChar <= Right(0);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_FIRST_RIGHT;

--WAIT_AFTER_FIRST_RIGHT-----
when WAIT_AFTER_FIRST_RIGHT =>
    if (txComplete = ACTIVE) then
        nextButtonState <= TRANSMIT_SECOND_RIGHT;
    else
        nextButtonState <= WAIT_AFTER_FIRST_RIGHT;
    end if;

--TRANSMIT_SECOND_RIGHT-----
when TRANSMIT_SECOND_RIGHT =>
    buttonChar <= Right(1);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_SECOND_RIGHT;

--WAIT_AFTER_SECOND_RIGHT-----
when WAIT_AFTER_SECOND_RIGHT =>
    if (txComplete = ACTIVE) then
        nextButtonState <= TRANSMIT_THIRD_RIGHT;
    else
        nextButtonState <= WAIT_AFTER_SECOND_RIGHT;
    end if;

--TRANSMIT_THIRD_RIGHT-----
when TRANSMIT_THIRD_RIGHT =>
    buttonChar <= Right(2);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_THIRD_RIGHT;

--WAIT_AFTER_THIRD_RIGHT-----
when WAIT_AFTER_THIRD_RIGHT =>
    if (txComplete = ACTIVE) then

```

```

        nextButtonState <= TRANSMIT_FOURTH_RIGHT;
    else
        nextButtonState <= WAIT_AFTER_THIRD_RIGHT;
    end if;

--TRANSMIT_FOURTH_RIGHT-----
when TRANSMIT_FOURTH_RIGHT =>
    buttonChar <= Right(3);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_FOURTH_RIGHT;

--WAIT_AFTER_FOURTH_RIGHT-----
when WAIT_AFTER_FOURTH_RIGHT =>
    if (txComplete = ACTIVE) then
        nextButtonState <= TRANSMIT_FIFTH_RIGHT;
    else
        nextButtonState <= WAIT_AFTER_FOURTH_RIGHT;
    end if;

--TRANSMIT_FIFTH_RIGHT-----
when TRANSMIT_FIFTH_RIGHT =>
    buttonChar <= Right(4);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_FIFTH_RIGHT;

--WAIT_AFTER_FIFTH_RIGHT-----
when WAIT_AFTER_FIFTH_RIGHT =>
    if (txComplete = ACTIVE) then
        nextButtonState <= TRANSMIT_SIXTH_RIGHT;
    else
        nextButtonState <= WAIT_AFTER_FIFTH_RIGHT;
    end if;

--TRANSMIT_SIXTH_RIGHT-----
when TRANSMIT_SIXTH_RIGHT =>
    buttonChar <= Right(5);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_SIXTH_RIGHT;

--WAIT_AFTER_SIXTH_RIGHT-----
when WAIT_AFTER_SIXTH_RIGHT =>
    if (txComplete = ACTIVE) then
        nextButtonState <= CHECK_CENTER_BUTTON;
    else
        nextButtonState <= WAIT_AFTER_SIXTH_RIGHT;
    end if;

--CHECK_CENTER_BUTTON-----
when CHECK_CENTER_BUTTON =>
    if (centerButtonSync = ACTIVE) then
        nextButtonState <= TRANSMIT_FIRST_CENTER;
    else
        nextButtonState <= BUTTON_TX_FINISHED;
    end if;

--TRANSMIT_FIRST_CENTER-----
when TRANSMIT_FIRST_CENTER =>

```

```

buttonChar <= Center(0);
buttonTxEn <= ACTIVE;
nextButtonState <= WAIT_AFTER_FIRST_CENTER;

--WAIT_AFTER_FIRST_CENTER-----
when WAIT_AFTER_FIRST_CENTER =>
    if (txComplete = ACTIVE) then
        nextButtonState <= TRANSMIT_SECOND_CENTER;
    else
        nextButtonState <= WAIT_AFTER_FIRST_CENTER;
    end if;

--TRANSMIT_SECOND_CENTER-----
when TRANSMIT_SECOND_CENTER =>
    buttonChar <= Center(1);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_SECOND_CENTER;

--WAIT_AFTER_SECOND_CENTER-----
when WAIT_AFTER_SECOND_CENTER =>
    if (txComplete = ACTIVE) then
        nextButtonState <= TRANSMIT_THIRD_CENTER;
    else
        nextButtonState <= WAIT_AFTER_SECOND_CENTER;
    end if;

--TRANSMIT_THIRD_CENTER-----
when TRANSMIT_THIRD_CENTER =>
    buttonChar <= Center(2);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_THIRD_CENTER;

--WAIT_AFTER_THIRD_CENTER-----
when WAIT_AFTER_THIRD_CENTER =>
    if (txComplete = ACTIVE) then
        nextButtonState <= TRANSMIT_FOURTH_CENTER;
    else
        nextButtonState <= WAIT_AFTER_THIRD_CENTER;
    end if;

--TRANSMIT_FOURTH_CENTER-----
when TRANSMIT_FOURTH_CENTER =>
    buttonChar <= Center(3);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_FOURTH_CENTER;

--WAIT_AFTER_FOURTH_CENTER-----
when WAIT_AFTER_FOURTH_CENTER =>
    if (txComplete = ACTIVE) then
        nextButtonState <= TRANSMIT_FIFTH_CENTER;
    else
        nextButtonState <= WAIT_AFTER_FOURTH_CENTER;
    end if;

--TRANSMIT_FIFTH_CENTER-----
when TRANSMIT_FIFTH_CENTER =>
    buttonChar <= Center(4);

```

```

        buttonTxEn <= ACTIVE;
        nextButtonState <= WAIT_AFTER_FIFTH_CENTER;

--WAIT_AFTER_FIFTH_CENTER-----
when WAIT_AFTER_FIFTH_CENTER =>
    if (txComplete = ACTIVE) then
        nextButtonState <= TRANSMIT_SIXTH_CENTER;
    else
        nextButtonState <= WAIT_AFTER_FIFTH_CENTER;
    end if;

--TRANSMIT_SIXTH_CENTER-----
when TRANSMIT_SIXTH_CENTER =>
    buttonChar <= Center(5);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_SIXTH_CENTER;

--WAIT_AFTER_SIXTH_CENTER-----
when WAIT_AFTER_SIXTH_CENTER =>
    if (txComplete = ACTIVE) then
        nextButtonState <= TRANSMIT_SEVENTH_CENTER;
    else
        nextButtonState <= WAIT_AFTER_SIXTH_CENTER;
    end if;

--TRANSMIT_SEVENTH_CENTER-----
when TRANSMIT_SEVENTH_CENTER =>
    buttonChar <= Center(6);
    buttonTxEn <= ACTIVE;
    nextButtonState <= WAIT_AFTER_SEVENTH_CENTER;

--WAIT_AFTER_SEVENTH_CENTER-----
when WAIT_AFTER_SEVENTH_CENTER =>
    if (txComplete = ACTIVE) then
        nextButtonState <= BUTTON_TX_FINISHED;
    else
        nextButtonState <= WAIT_AFTER_SEVENTH_CENTER;
    end if;

--BUTTON_TX_FINISHED-----
when BUTTON_TX_FINISHED =>
    buttonTxFinished <= ACTIVE;
    nextButtonState <= WAIT_FOR_BUTTON_CONTROL;
end case;
end process BUTTON_STATE_TRANSITION;

--Latches for the Digits(enable signals comes from Ascii State Machine)--
-----\
--Digit1-----
DIGIT01_LATCH:process (reset, clock)
begin
    if (reset = ACTIVE) then
        digit1 <= (others => not ACTIVE);
    elsif (rising_edge(clock)) then
        if (digit01En = ACTIVE) then
            digit1 <= myChar(3 downto 0);
        end if;
    end if;
end process;

```

```

    end if;
end process DIGIT01_LATCH;

--Digit2-----
DIGIT02_LATCH:process (reset, clock)
begin
    if (reset = ACTIVE) then
        digit2 <= (others => not ACTIVE);
    elsif (rising_edge(clock)) then
        if (digit02En = ACTIVE) then
            digit2 <= myChar(3 downto 0);
        end if;
    end if;
end process DIGIT02_LATCH;

--Digit3-----
DIGIT03_LATCH:process (reset, clock)
begin
    if (reset = ACTIVE) then
        digit3 <= (others => not ACTIVE);
    elsif (rising_edge(clock)) then
        if (digit03En = ACTIVE) then
            digit3 <= myChar(3 downto 0);
        end if;
    end if;
end process DIGIT03_LATCH;

--Digit4-----
DIGIT04_LATCH:process (reset, clock)
begin
    if (reset = ACTIVE) then
        digit4 <= (others => not ACTIVE);
    elsif (rising_edge(clock)) then
        if (digit04En = ACTIVE) then
            digit4 <= myChar(3 downto 0);
        end if;
    end if;
end process DIGIT04_LATCH;

DIGIT_TO_NUM_CONVERT: process (digit1, digit2)
    variable onesDigit: integer range 0 to 9;
    variable tensDigit: integer range 0 to 9;
begin
    onesDigit := to_integer(unsigned(digit1));
    tensDigit := to_integer(unsigned(digit2));

    tensDigit := tensDigit * 10;
    userNum <= tensDigit + onesDigit;
end process DIGIT_TO_NUM_CONVERT;

--sets segDigits to the digits from the Ascii State Machine-----
SEG_REGISTER:process (reset, clock)
begin
    if (reset = ACTIVE) then
        segDigit3 <= (others => not ACTIVE);
        segDigit2 <= (others => not ACTIVE);
        segDigit1 <= (others => not ACTIVE);
    end if;
end process SEG_REGISTER;

```

```

        segDigit0 <= (others => not ACTIVE);
    elsif (rising_edge(clock)) then
        if (segEn = ACTIVE) then
            segDigit3 <= digit4;
            segDigit2 <= digit3;
            segDigit1 <= digit2;
            segDigit0 <= digit1;
        end if;
    end if;
end process SEG_REGISTER;

--Driver to turn LEDs on or off depending on userNum-----
LED_DRIVER: process (reset,clock)
    variable tempLeds: std_logic_vector(15 downto 0);
begin
    if (reset = ACTIVE) then
        leds <= (others => not ACTIVE);
        tempLeds := (others => not ACTIVE);
    elsif (rising_edge(clock)) then
        if (ledOnEn = ACTIVE) then
            tempLeds(userNum) := ACTIVE;
        elsif (ledOffEn = ACTIVE) then
            tempLeds(userNum) := not ACTIVE;
        end if;
        leds <= tempLeds;
    end if;
end process LED_DRIVER;

--Transmission Organizer to only send one char and enable line to
Transmitter----
charToSend <= buttonChar or switchChar;
txEn <= buttonTxEn or switchTxEn;

end SerialControl_ARCH;

```

Test Bench Code:

```
-----  
-- SerialControl_tb  
-- Sofiyan Monga  
--  
--      Testbench for SerialControl component. Apply certain inputs and  
control  
--      serialIn to determine correct performance of the receiver,  
transmitter, and  
--      the rest of the component.  
--  
-----
```

```
library ieee;  
use ieee.std_logic_1164.all;
```

```
entity SerialControl_tb is  
-- Port ( );  
end SerialControl_tb;
```

```
architecture SerialControl_tb_ARCH of SerialControl_tb is
```

```
    --constants-----  
    constant ACTIVE      : std_logic := '1';  
    constant CLOCK_FREQ: integer    := 100_000_000;  
    constant BAUD_RATE  : integer    := 115_200;  
    constant BIT_TIME   : time       := (1_000_000_000/BAUD_RATE) * 1 ns;
```

```
    --unit under test-----  
    component SerialControl  
        Port (  
            clock           : in std_logic;  
            rawReset        : in std_logic;  
            serialIn         : in std_logic;  
            upButton        : in std_logic;  
            leftButton       : in std_logic;  
            rightButton      : in std_logic;  
            centerButton     : in std_logic;  
            switches         : in std_logic_vector (15 downto 0);  
            leds             : out std_logic_vector (15 downto 0);  
            segments        : out std_logic_vector (6 downto 0);  
            anodes           : out std_logic_vector (3 downto 0);  
            serialOut        : out std_logic);  
    end component;
```

```
    --UUT signals-----  
    signal clock           : std_logic;  
    signal downButton      : std_logic;  
    signal rightButton     : std_logic;  
    signal leftButton      : std_logic;  
    signal centerButton    : std_logic;  
    signal upButton        : std_logic;  
    signal serialIn        : std_logic;  
    signal serialOut       : std_logic;  
    signal switches        : std_logic_vector(15 downto 0);
```

```

signal leds          : std_logic_vector(15 downto 0);
signal segments      : std_logic_vector(6  downto 0);
signal anodes         : std_logic_vector(3  downto 0);

begin
--unit-under-test-----
UUT: SerialControl port map (
    clock          => clock,
    rawReset       => downButton,
    leftButton     => leftButton,
    rightButton    => rightButton,
    centerButton   => centerButton,
    upButton       => upButton,
    serialIn       => serialIn,
    serialOut      => serialOut,
    switches       => switches,
    leds          => leds,
    segments       => segments,
    anodes         => anodes);

--clock-definition-----
SYS_CLOCK: process
begin
    clock <= not ACTIVE;
    wait for 5 ns;
    clock <= ACTIVE;
    wait for 5 ns;
end process SYS_CLOCK;

--reset-driver-----
SYS_RESET: process
begin
    downButton <= ACTIVE;
    wait for 15 ns;
    downButton <= not ACTIVE;
    wait;
end process SYS_RESET;

--input-driver-----
INPUT_DRIVER: process
begin
--initialize inputs to zero-----
    switches <= (others => not ACTIVE);
    upButton <= not ACTIVE;
    centerButton <= not ACTIVE;
    leftButton <= not ACTIVE;
    rightButton <= not ACTIVE;

--set serial line to idle-----
    serialIn <= '1';
    wait for 316 ns;

--transmit 'L'-----01001100-----
    serialIn <= '0';
    wait for BIT_TIME;

    serialIn <= '0';

```

```

wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;

serialIn <= '1';
wait for BIT_TIME;

--transmit first digit for 'L'-----00110001-----
serialIn <= '0';
wait for BIT_TIME;

serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;

serialIn <= '1';
wait for BIT_TIME;

--transmit second digit for 'L'-----00110010-----
serialIn <= '0';
wait for BIT_TIME;

serialIn <= '0';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;

```

```
serialIn <= '1';  
wait for BIT_TIME;  
serialIn <= '0';  
wait for BIT_TIME;  
serialIn <= '0';  
wait for BIT_TIME;
```

```
serialIn <= '1';  
wait for BIT_TIME;
```

```
--transmit 'M'-----01001101-----  
serialIn <= '0';  
wait for BIT_TIME;
```

```
serialIn <= '1';  
wait for BIT_TIME;  
serialIn <= '0';  
wait for BIT_TIME;  
serialIn <= '1';  
wait for BIT_TIME;  
serialIn <= '1';  
wait for BIT_TIME;  
serialIn <= '0';  
wait for BIT_TIME;  
serialIn <= '0';  
wait for BIT_TIME;  
serialIn <= '1';  
wait for BIT_TIME;  
serialIn <= '0';  
wait for BIT_TIME;
```

```
serialIn <= '1';  
wait for BIT_TIME;
```

```
--transmit first digit for 'M'-----00110001-----  
serialIn <= '0';  
wait for BIT_TIME;
```

```
serialIn <= '1';  
wait for BIT_TIME;  
serialIn <= '0';  
wait for BIT_TIME;  
serialIn <= '0';  
wait for BIT_TIME;  
serialIn <= '0';  
wait for BIT_TIME;  
serialIn <= '1';  
wait for BIT_TIME;  
serialIn <= '1';  
wait for BIT_TIME;  
serialIn <= '0';  
wait for BIT_TIME;  
serialIn <= '0';  
wait for BIT_TIME;
```

```

serialIn <= '1';
wait for BIT_TIME;

--transmit second digit for 'M'-----00110010-----
serialIn <= '0';
wait for BIT_TIME;

serialIn <= '0';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;

serialIn <= '1';
wait for BIT_TIME;

--transmit 'D'-----01000100-----
serialIn <= '0';
wait for BIT_TIME;

serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;

serialIn <= '1';
wait for BIT_TIME;

--transmit first digit for 'D'-----00110001-----
serialIn <= '0';

```

```

wait for BIT_TIME;

serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;

serialIn <= '1';
wait for BIT_TIME;

--transmit second digit for 'D'-----00110010-----
serialIn <= '0';
wait for BIT_TIME;

serialIn <= '0';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;

serialIn <= '1';
wait for BIT_TIME;

--transmit third digit for 'D'-----00110011-----
serialIn <= '0';
wait for BIT_TIME;

serialIn <= '1';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';

```

```

wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;

serialIn <= '1';
wait for BIT_TIME;

--transmit fourth digit for 'D'-----00110100-----
serialIn <= '0';
wait for BIT_TIME;

serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;

serialIn <= '1';
wait for BIT_TIME;

--transmit 'B' after pushing buttons-----01000010-----
upButton <= ACTIVE;
leftButton <= ACTIVE;

serialIn <= '0';
wait for BIT_TIME;

serialIn <= '0';
wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;
serialIn <= '0';

```

```

wait for BIT_TIME;
serialIn <= '1';
wait for BIT_TIME;
serialIn <= '0';
wait for BIT_TIME;

serialIn <= '1';
wait for BIT_TIME;

--transmit 'S' after activating one of the switches-----01010011---
--    switches <= "0000000000000001";

--    serialIn <= '0';
--    wait for BIT_TIME;

--    serialIn <= '1';
--    wait for BIT_TIME;
--    serialIn <= '1';
--    wait for BIT_TIME;
--    serialIn <= '0';
--    wait for BIT_TIME;
--    serialIn <= '0';
--    wait for BIT_TIME;
--    serialIn <= '1';
--    wait for BIT_TIME;
--    serialIn <= '0';
--    wait for BIT_TIME;
--    serialIn <= '1';
--    wait for BIT_TIME;
--    serialIn <= '0';
--    wait for BIT_TIME;

--    serialIn <= '1';
--    wait for BIT_TIME;

--    --transmit first digit for 'S'-----00110000-----
--    serialIn <= '0';
--    wait for BIT_TIME;

--    serialIn <= '0';
--    wait for BIT_TIME;
--    serialIn <= '0';
--    wait for BIT_TIME;
--    serialIn <= '0';
--    wait for BIT_TIME;
--    serialIn <= '0';
--    wait for BIT_TIME;
--    serialIn <= '1';
--    wait for BIT_TIME;
--    serialIn <= '1';
--    wait for BIT_TIME;
--    serialIn <= '0';
--    wait for BIT_TIME;
--    serialIn <= '0';

```

```

--      wait for BIT_TIME;

--      serialIn <= '1';
--      wait for BIT_TIME;

--      --transmit second digit for 'S'-----00110000-----
--      serialIn <= '0';
--      wait for BIT_TIME;

--      serialIn <= '0';
--      wait for BIT_TIME;
--      serialIn <= '0';
--      wait for BIT_TIME;
--      serialIn <= '0';
--      wait for BIT_TIME;
--      serialIn <= '0';
--      wait for BIT_TIME;
--      serialIn <= '1';
--      wait for BIT_TIME;
--      serialIn <= '1';
--      wait for BIT_TIME;
--      serialIn <= '0';
--      wait for BIT_TIME;
--      serialIn <= '0';
--      wait for BIT_TIME;

--      serialIn <= '1';
--      wait for BIT_TIME;

      wait;
end process INPUT_DRIVER;

end SerialControl_tb_ARCH;

```